

[Home](#)

[PCB Blog](#) ▾

[Design & Technology](#) ▾

[Log In](#)



[Search](#)

[AllElectroHub](#) > [Analog & Power Technology](#) > [Crystal Oscillator Operation and Load Capacitor Selection](#)
Industry & Applications ▾

Capacitor Selection

Industry & Applications ▾

Author : Adrian September 24, 2025

Table of Contents

[Preface](#)

[Quartz Crystal Characteristics and Equivalent Model](#)

[Example: Adjusting External Parameters for an 8 MHz Crystal](#)

[Oscillator Principle](#)

[Pierce Oscillator](#)


[Pierce Oscillator Design](#)

Preface

Most designers are familiar with Pierce topology oscillators, but few fully understand how they work or how to design them correctly. Oscillator issues are often overlooked until production, causing delays or operational problems. Oscillators should receive appropriate attention during the design phase and before production.

Quartz Crystal Characteristics and Equivalent Model

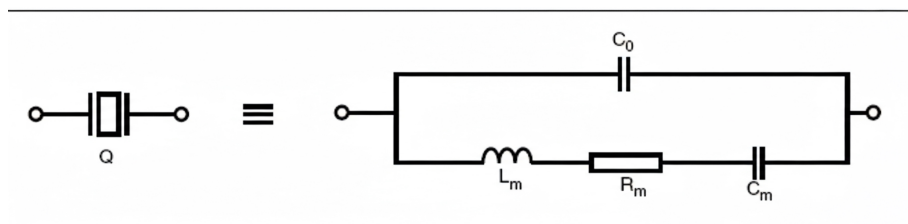A quartz crystal is a piezoelectric device that converts electrical energy to mechanical energy and vice versa at its resonance frequency. It can be represented by the following equivalent circuit:



The crystal impedance can be expressed by the following equation (assuming R_m is negligible):

$$Z = \frac{j}{\omega} \times \frac{\omega^2 L_m C_m - 1}{(C_0 + C_m) - \omega^2 L_m C_m C_0} \quad (1)$$

F_s is the series resonance frequency where reactance $Z = 0$ (it is the resonance of the L_m , C_m and R_m branch). Its expression is:

$$F_s = \frac{1}{2\pi\sqrt{L_m C_m}} \quad (2)$$

The range from F_s to F_a is commonly called the parallel-resonance region (shaded in the figure). In this region the crystal operates in parallel resonance (this is the normal operating region; $F_a > F_s$ is the bandwidth. Narrower bandwidth implies higher Q and more stable oscillation frequency). In this region the crystal presents an inductive characteristic, producing approximately 180° phase shift. The oscillation frequency F_P (also called F_L : load frequency) is given by:


From this expression, it is clear that the oscillation frequency can be tuned by adjusting the load capacitance CL. This is why crystal vendors specify an external load capacitance CL in their datasheets. Specifying CL ensures the crystal oscillates at its nominal frequency.

Example: Adjusting External Parameters for an 8 MHz Crystal

Using the previous expressions, the crystal's F_s , F_a and F_P were calculated as: $F_s = 7,988,768$ Hz, $F_a = 8,008,102$ Hz. If the crystal's CL is 10 pF, the oscillation frequency is $F_P = 7,995,695$ Hz. To reach the 8 MHz nominal frequency, CL should be 4.02 pF.

Oscillator Principle

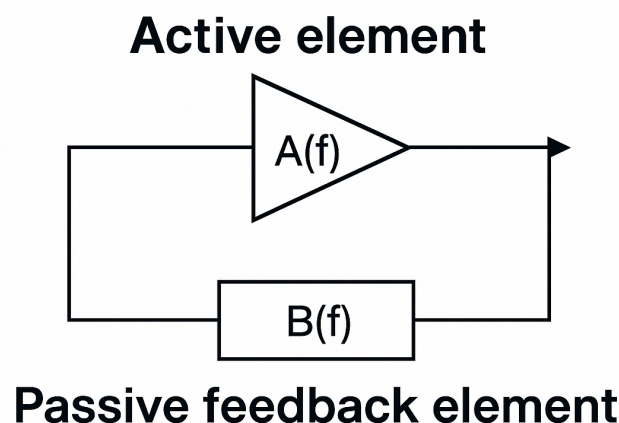An oscillator consists of an amplifier and a feedback network that provides frequency selection. The block diagram illustrates the basic principle:



- $A(f)$ is the amplifier section, which supplies energy to sustain oscillation.
- $B(f)$ is the feedback path, which determines the oscillation frequency.

To start oscillation, the Barkhausen conditions must be met: the closed-loop gain should be greater than 1 and the total phase shift should be 360° .


$$|A(f)| \cdot |B(f)| \geq 1 \text{ and } \alpha(f) + \beta(f) = 2\pi$$

To sustain oscillation, ensure $|A(f)| \cdot |B(f)| \gg 1$. This implies the open-loop gain should be much greater than 1; the time to reach steady oscillation depends on that open-loop gain.

However, satisfying these conditions alone does not explain how a crystal oscillator starts. A startup energy source is also required. In practice, power-up transients and noise provide the necessary energy. The startup energy must be sufficient to excite oscillation at the desired frequency.

The amplifier in this condition is unstable, so any disturbance in the positive feedback loop can trigger oscillation. Disturbances can come from power-up events, device enable/disable actions, crystal thermal noise, and so on. Note that only noise components within the crystal's operating frequency

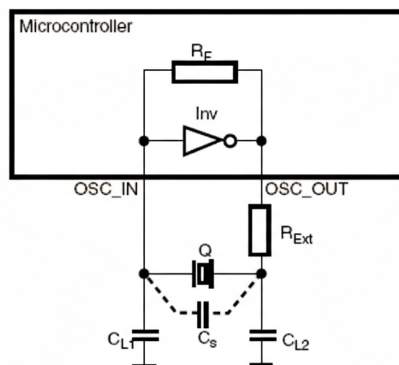The Pierce oscillator is common due to its low power, low cost and good stability.




- Inv: internal inverter acting as the amplifier.
- Q: quartz or ceramic resonator.
- R_F : internal feedback resistor. Its presence biases the inverter into the linear region so it provides gain equivalent to an amplifier.
- R_{Ext} : external current-limiting resistor.
- C_{L1} and C_{L2} : two external load capacitors.
- C_s : stray capacitance from PCB traces and connections at OSC_IN and OSC_OUT pins.

Pierce Oscillator Design

Feedback Resistor R_F

In many cases R_F is embedded inside the oscillator circuit (for example, inside many microcontrollers). Its role is to introduce feedback that makes the inverter operate as an amplifier.

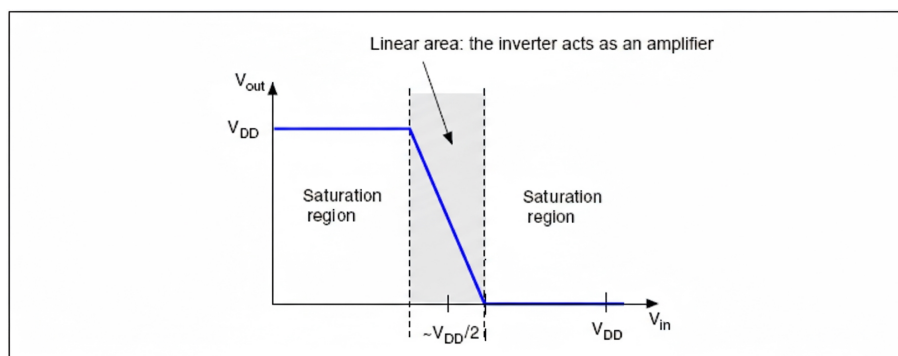The feedback resistor between V_{in} and V_{out} biases the inverter when $V_{out} = V_{in}$, forcing the inverter to operate in its linear region (shaded area in the figure). The amplifier then amplifies noise within the crystal's parallel-resonance region (e.g. crystal thermal noise), which triggers startup. In some cases, after startup the oscillator may continue to run even if R_F is removed.



Load Capacitance C_L

Load capacitance C_L refers to the effective capacitance seen by the crystal. C_L depends on the external capacitors C_{L1} and C_{L2} and the PCB stray capacitance C_s . The crystal manufacturer specifies

specified value. The effective CL is:

Industry & Applications ▾

$$C_L = \frac{C_{L1} \times C_{L2}}{C_{L1} + C_{L2}} + C_s$$

Example calculation for CL1 and CL2: if CL = 15 pF and assume Cs = 5 pF, then:

$$C_L - C_s = \frac{C_{L1} \times C_{L2}}{C_{L1} + C_{L2}} = 10 \text{ pF}$$

Thus CL1 = CL2 = 20 pF.

Gain Margin of the Oscillator

Gain margin is a key parameter that determines whether the oscillator will reliably start.

Where:

- gm is the inverter transconductance, in mA/V for high frequency or μA/V for low frequency (e.g. 32 kHz).
- gmcrit (critical gm) depends on the crystal parameters. Assuming CL1 = CL2 and that the crystal sees the manufacturer-specified CL, gmcrit is:

ESR is the crystal equivalent series resistance. According to the theory by Eric A. Vittoz et al. (see "High-Performance Crystal Oscillator Circuits: Theory and Application", IEEE Journal of Solid-State Circuits, vol. 23, No. 3, pp. 774-782, Jun. 1988), the impedances of the amplifier and the two external capacitors compensate the reactance of the crystal's RLC dynamic equivalent circuit.

To satisfy startup conditions, the inverter transconductance must meet $gm > gmcrit$.



0



0

Share ·  ·  ·  · 


Recommended Reading



China SiC Substrate Prices Fall in 2024; 800V Adoption Nears

September 24, 2025

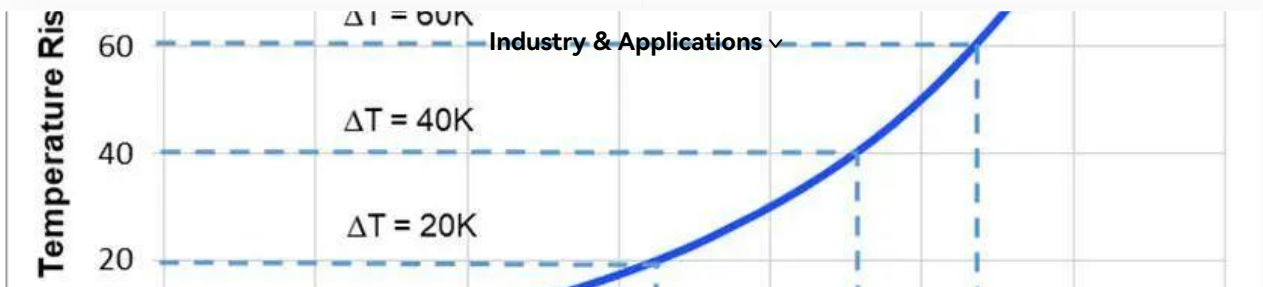Analysis of China SiC substrate price decline in 2024: domestic prices plunged vs global quotes, driven by capacity




How to Choose Inductors: Common Parameters

September 24, 2025

Technical guide to inductors and inductance: covers permeability, resistance, core loss, saturation, self-resonant frequency, ripple and selection for DC/DC converters.

Article

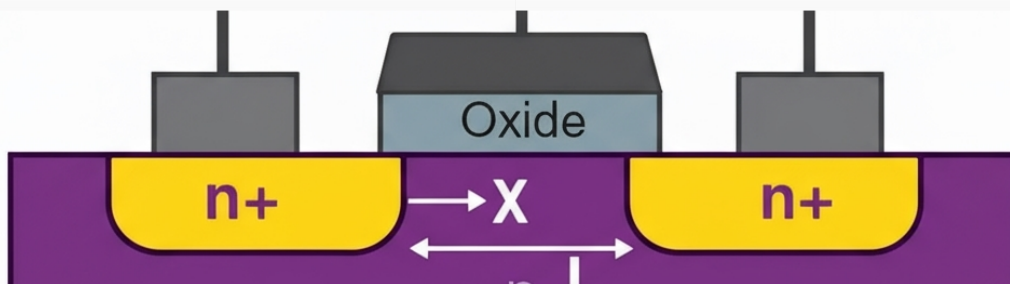

MOSFET Gate Driver Circuit Design

September 24, 2025

Overview of MOSFET gate drive principles, gate-to-source capacitance and gate charge, threshold behavior, and gate charge calculation for driver circuit design.

Article




Understanding MOSFET Parameters

September 23, 2025

MOSFET technical summary of electrical and thermal specs: key ratings (V_{DS} , V_{GS} , I_D), thermal resistance $R_{\theta JA}$ and T_j calculation, capacitances, gate charge and switching timings.

Article

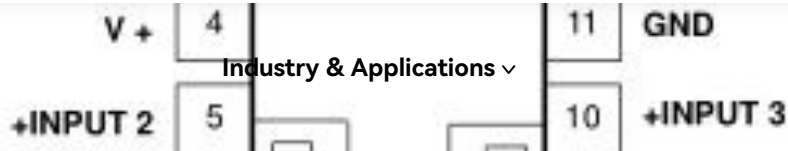[Home](#)[PCB Blog](#) ▾[Design & Technology](#) ▾[Log In](#) [Sign Up](#)[Industry & Applications](#) ▾

Handling Unused Op Amp or Comparator Pins

September 23, 2025

Guidance on terminating unused op amp sections and comparators to avoid floating inputs: use voltage followers to set inputs to ground or $V_{CC}/2$.

Article



Silicon Carbide Power Devices: Properties and Principles

September 23, 2025

Review of silicon carbide (SiC) power devices covering principles, key characteristics, applications and challenges for high-efficiency power electronics and energy conversion.

Article

Get Instant PCB Quotations

Full-featured PCB manufacturing service at low cost.

Dimensions

100



X

100



mm

Layer

2 Layers

Quantity

5

 [Quote Now](#)



[Home](#)

[PCB Blog](#) ▾

[Design & Technology](#) ▾

[Log In](#) 

[Sign Up](#)

Follow Us



– Free Shipping Worldwide

Industry & Applications

PCB Design

PCB Knowledge

PCB Assembly

PCB Ordering

Embedded Systems

Analog & Power Technology

Wireless & RF Design

Sensors & MEMS

Microcontrollers & Control

Memory & Storage Technology

EMC/EMI & Signal Integrity

EDA & IC Design

Automotive Electronics

Medical Electronics

Industrial Automation & Control

Smart Grid & New Energy

IoT Applications

Wearable & Portable Devices

Communication & 5G

AI & Edge Computing

